

**BENGKEL KOMPONEN MAGNETIK
DAN ELEKTRONIKA DAYA
HALF-BRIDGE DC-DC CONVERTER**

Dosen: Ir. Moh.Zaenal Efendi, MT.



Oleh :

Muhammad Fauqi Asyraf

(1310181058)

3 D4 Teknik Elektro Industri B

**PROGRAM STUDI D4 TEKNIK ELEKTRO INDUSTRI
DEPARTEMEN TEKNIK ELEKTRO
POLITEKNIK ELEKTRONIKA NEGERI SURABAYA
2020/2021**

PROJECT WORK HALF-BRIDGE DC-DC CONVERTER 2021 (UNTUK NRP GENAP)

The Half-Bridge DC-DC Converter has following parameters :

$V_s = 100$ Volt

$V_o = 19$ Volt

$I_o = 3$ A

Duty cycle = 0.4

Switching Frekuensi (f_s) = 40 kHz

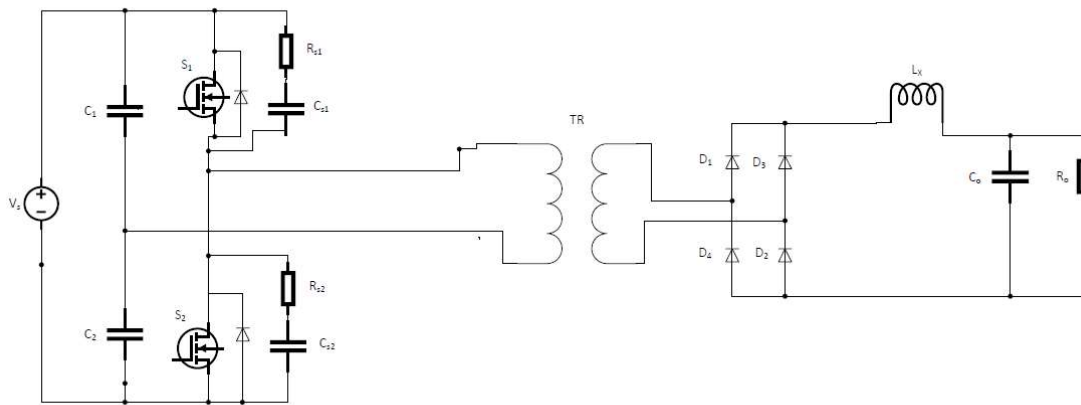


Figure 1. Half-Bridge DC-DC Converter Circuit
(created with Microsoft Visio app)

Component:

$S_1 = S_2$: MOSFET IRFP460($t_f=75$ ns based on datasheet)

$C_1 = C_2$: 470uF, 400 Volt

$D_1 = D_2 = D_3 = D_4$: MUR 1560 (Ultra Fast Recovery Diode) $V_f = 1.5$ volt(based on datashet MUR1560)

Inductor (L_x) : Ferrit Core PQ 3230 with Cross sectional are ($A_c=1.61\text{cm}^2$);

Bobbin diameter ($D_{bob1} = 16$ mm)

Transformer (TR) : Ferrit Core PQ 3535 with Cross sectional are ($A_c=1.96\text{cm}^2$);

Bobbin diameter ($D_{bob2} = 17$ mm)

C_o : Output capacitor (Calculation), 50 Volt

$R_{s1} = R_{s1}$: Snubber resistor (470Ω , 10 watt)

$C_{s1} = C_{s1}$: Snubber capacitor (10nf, 1 kVolt)

SOLUTION:

A. HIGH FREQUENCY INDUCTOR DESIGN

- **Output Voltage:**

$$V_o = V_{in} \times \frac{N_2}{N_1} \times D$$

$$19 = 100 \times \frac{N_2}{N_1} \times 0.4$$

$$\frac{N_2}{N_1} = \frac{19}{40} = 0.475$$

$$\frac{N_1}{N_2} = \frac{40}{19} = 2.1$$

- **Filter inductor**

$$L_x = \frac{1}{\Delta i L_x} \times (V_{in(a)} - V_o) \times \left(\frac{1}{2f_s} \right) \times \left(\frac{V_o + 2V_f}{V_{in} + 2V_f} \right)$$

Where:

$$V_{in(a)} = \frac{V_{in}}{2 \times \frac{N_1}{N_2} - 2V_F}$$

$$V_{in(a)} = \frac{100}{2 \times 2.1 - 2(1.5)} = \frac{100}{4.2 - 3} = 82.61 \text{ volt}$$

$$\Delta i L_x = 20\% \times I_o$$

$$\Delta i L_x = 20\% \times 3$$

$$\Delta i L_x = 0.6 \text{ A}$$

$$L_x = \frac{1}{0.6} \times (82.61 - 19) \times \left(\frac{1}{80 \times 10^3} \right) \times \left(\frac{19 + 2(1.5)}{100 + 2(1.5)} \right)$$

$$L_x = 2.8305 \times 10^{-4} \text{ H} \approx 284 \mu\text{H}$$

- **The maximum inductor current**

$$i_{L(max)} = i_{L(avg)} + \frac{\Delta i L_x}{2}$$

$$i_{L(avg)} = \frac{V_o}{R} = I_o$$

$$I_o = \frac{V_o}{R} = i_{L(avg)} = 3 \text{ A}$$

$$i_{L(max)} = 3 + \frac{0.6}{2}$$

$$i_{L(max)} = 3.3 \text{ A}$$

- **Winding number of inductor**

$$n = \frac{L \times i_{L(max)}}{B_{max} \times A_c} \times 10^4; B_{max} = 0.25 \text{ T}, A_c = 1.61 \text{ cm}^2$$

$$n = \frac{2.8305 \times 10^{-4} \times 3.3}{0.25 \times 1.61} \times 10^4$$

$$n = 23.21$$

$$n \approx 24 \text{ turns}$$

- **Wire size is based on RMS current of inductor**

$$i_{L(rms)t} = \sqrt{i_{L(avg)}^2 + \left(\frac{\Delta i_L / 2}{\sqrt{3}}\right)^2}$$

$$i_{L(rms)t} = \sqrt{(3)^2 + \left(\frac{0.3}{\sqrt{3}}\right)^2}$$

$$i_{L(rms)t} = \sqrt{9 + (0.173)^2}$$

$$i_{L(rms)t} = \sqrt{9 + 0.03}$$

$$i_{L(rms)t} = \sqrt{9.03} = 3.01 \text{ A}$$

- **Calculation of Wire Size**

➤ Cross sectional Area of Wire(qw)

$$q_{w(L)} = \frac{i_{L(rms)t}}{J}; J = 4.5 \text{ A/mm}^2 \text{ (current density)}$$

$$q_{w(L)} = \frac{3.01}{4.5} = 0.67 \text{ mm}^2$$

➤ Recalculate by assuming number of split wire(Σ split)=10?

$$i_{L(rms)split} = \frac{i_{L(rms)t}}{\Sigma \text{split}_L} = \frac{3.005}{10} = 0.3$$

$$q_{w(L)split} = \frac{i_{L(rms)split}}{J} = \frac{0.3}{3.4} = 0.066 \text{ mm}^2$$

$$d_{w(L)split} = \sqrt{\frac{4}{\pi} \times q_{w(L)split}} \text{ mm}$$

$$d_{w(L)split} = \sqrt{1.27 \times 0.066} = \sqrt{0.0838} = 0.289 \text{ mm}$$

- Recalculate split based on choosen wire diameter(0.3mm)

$$d_{w(L)split} = \sqrt{\frac{4}{\pi} \times q_{w(L)split}} \text{ mm}^2$$

$$0.3 = \sqrt{\frac{4}{\pi} \times q_{w(L)split}}$$

$$0.09 = 1.273 \times q_{w(L)split}$$

$$q_{w(L)split} = \frac{0.09}{1.273} = 0.07$$

$$q_{w(L)split} = \frac{i_{L(rms)split}}{J}$$

$$i_{L(rms)split} = J \times q_{w(L)split}$$

$$i_{L(rms)split} = 0.07 \times 4,5 = 0,315 \text{ A}$$

$$i_{L(rms)split} = \frac{i_{L(rms)split}}{\Sigma split_L}$$

$$\Sigma split_L = \frac{i_{L(rms)t}}{i_{L(rms)split}} = \frac{3.01}{0.315} = 9.6 \approx 10 \text{ split}$$

- **Wire size**

Diameter of bobbin PQ3230(D_{bob1})=16mm=1.6cm

Circumference of Bobin(K_{bob1}) = $\pi \times D_{bob1}$

Circumference of Bobin = $\pi \times 1.6 = 5.024 \text{ cm}$

Total Wire Length = $(n_{(winding)} \times K_{bob1} \times \Sigma split_L) + 0.4 (n_{(winding)} \times K_{bob1} \times \Sigma split_L)$

Total Wire Length = $(24 \times 5.024 \times 10) + 40\% \times (24 \times 0.24 \times 10)$

Total Wire Length = $(1205,76) + 40\% \times (653.12) = 1688 \text{ cm} \approx 17 \text{ m}$

- **Air Gap Length**

$$l_g = \frac{\mu_o \times L_x \times I_{max}^2}{B_{max}^2 \times A_c} \times 10^4$$

$$l_g = \frac{4\pi \times 10^{-7} \times 284 \times 10^{-6} \times 3.3^2}{0.25^2 \times 1.61} \times 10^4$$

$$l_g = 0.0004 \text{ m} = 0.4 \text{ mm} =$$

B. HIGH FREQUENCY TRANSFORMER DESIGN

- Output Voltage:

$$V_o = V_{in} \times \frac{N_2}{N_1} \times D$$

$$19 = 100 \times \frac{N_2}{N_1} \times 0.4$$

$$\frac{N_2}{N_1} = \frac{19}{40} = 0.475$$

$$\frac{N_1}{N_2} = \frac{40}{19} = 2.1$$

- Number of primary winding:

$$N_{1(min)} = \frac{D \times T \times V_{in}}{2 \times B_{max} \times A_c} \times 10^4 \quad B_{max} = 0.25 \text{ Tesla}; A_c = 1.96 \text{ in cm}^2$$

$$T = \frac{1}{f} = \frac{1}{40k} = 0.000025 \text{ s}$$

$$N_{1(min)} = \frac{0.4 \times 2.5 \times 10^{-5} \times 100}{2 \times 0.25 \times 1.96} \times 10^4$$

$$N_{1(min)} = 10.2 \text{ turns}$$

$$N_1 = 2 \times N_{1(min)}$$

$$N_1 = 2 \times 10.2 = 20.4 \approx 21 \text{ turns}$$

- Number of secondary winding:

$$N_2 = n \times N_1; n = \text{transformer ratio}$$

$$N_2 = \frac{19}{40} \times 20.4$$

$$N_2 = 9.69 \approx 10 \text{ turns}$$

- RMS Primary Current:

$$I_{1,rms} = \frac{N_2}{N_1} \times I_o \times \sqrt{D}$$

$$I_{1,rms} = \frac{19}{40} \times 3 \times \sqrt{0.4}$$

$$I_{1,rms} = 0.9 \text{ A}$$

- **Primary wire size**

$$s = 4.5 \text{ A/mm}^2$$

$$d_1 = \sqrt{\frac{4 \times I_{1,rms}}{\pi \times s}}$$

$$d_1 = \sqrt{\frac{4 \times 0.9}{\pi \times 4.5}}$$

$$d_1 = 0.51 \text{ mm}$$

- **Σ Split primary Winding calculation based on chosen wire size(0.4 mm)**

$$d_{w(p)split} = 0.4 \text{ mm}$$

$$d_{w(p)split} = \sqrt{\frac{4 \times q_{w(p)split}}{\pi}}$$

$$0.4 = \sqrt{\frac{4 \times q_{w(p)split}}{3.14}}$$

$$0.16 = \frac{4 \times q_{w(p)split}}{3.14}$$

$$0.5 = 4 \times q_{w(p)split}$$

$$q_{w(p)split} = 0.125 \text{ mm}^2$$

$$i_{1(rms)split} = J \times q_{w(p)split}$$

$$0.125 = \frac{i_{1(rms)split}}{4.5}$$

$$i_{1(rms)split} = 1.25 \times 4.5 = 0.5625 \text{ A}$$

$$i_{1(rms)split} = \frac{i_{1(rms)}}{\Sigma \text{Split}_p}$$

$$\Sigma \text{Split}_p = \frac{i_{1(rms)}}{i_{1(rms)split}} = \frac{0.9}{0.5625} = 1.6 \approx 2 \text{ split}$$

- **RMS secondary current:**

$$I_{2,rms} = \frac{1}{2} \times I_o \times \sqrt{1 + D}$$

$$I_{2,rms} = \frac{1}{2} \times 3 \times \sqrt{1.4}$$

$$I_{2,rms} = 1.77 \text{ A}$$

- **Secondary wire size**

$$d_2 = \sqrt{\frac{4 \times I_{2,rms}}{\pi \times s}}$$

$$d_2 = \sqrt{\frac{4 \times 1.77}{\pi \times 4.5}}$$

$$d_2 = 0.71 \text{ mm}$$

- **Σ Split secondary Winding calculation based on choosen wire size(0.4 mm)**

$$d_{w(s)split} = 0.4 \text{ mm}$$

$$d_{w(s)split} = \sqrt{\frac{4 \times q_{w(s)split}}{\pi}}$$

$$0.4 = \sqrt{\frac{4 \times q_{w(s)split}}{3.14}}$$

$$0.16 = \frac{4 \times q_{w(s)split}}{3.14}$$

$$0.5 = 4 \times q_{w(s)split}$$

$$q_{w(s)split} = 0.125 \text{ mm}^2$$

$$q_{w(s)split} = \frac{i_{2(rms)split}}{J}$$

$$0.125 = \frac{i_{2(rms)split}}{4.5}$$

$$i_{2(rms)split} = 1.25 \times 4.5 = 0.5625 \text{ A}$$

$$i_{2(rms)split} = \frac{i_{2(rms)}}{\Sigma Split_s}$$

$$\Sigma Split_s = \frac{i_{2(rms)}}{i_{2(rms)split}} = \frac{1.77}{0.5625} = 3.14 \approx 4 \text{ split}$$

- **Induktor magnitasi(L_m)**

$$L_m = \frac{V_{c1} \times D \times T}{20\% \times (i_1 + \frac{N_2}{N_1} \times i_2)}$$

$$L_m = \frac{50 \times 0.4 \times 2.5 \times 10^{-5}}{20\% \times \left(0.9 + \frac{19}{40} \times 1.77\right)}$$

$$L_m = \frac{50 \times 10^{-5}}{20\% \times (1.425 + 0.475 \times 1.77)}$$

$$L_m = \frac{50 \times 10^{-5}}{0.45} = 111 \times 10^{-5} = 11.1 \mu H$$

- **Split Pattern**

2 split primer

4 split sekunder

additional = 1split primer+2split sekunder

pattern:

P1S1S2 P2S3S4 **P3S5S6**

Split 1 split 2 **additional**

- **Length of wire**

Diameter of bobbin PQ3535(D_{bob2})=17 mm=1.7 cm

Circumference of Bobbin (K_{bob2}) = $\pi \times D_{bob2}$ = 1.7×3.14=5.338 cm

$$P_p = (N_p \times K_{bob2} \times \Sigma Split_p) + 0.3 (N_p \times K_{bob2} \times \Sigma Split_p)$$

$$P_p = (20.4 \times 5.338 \times 2) + 0.3(20.4 \times 5.338 \times 2)$$

$$P_p = 21.8 + 65.33 = 283.13 \text{ cm} \approx 2.9 \text{ m}$$

$$P_s = (N_s \times K_{bob2} \times \Sigma Split_s) + 0.3 (N_s \times K_{bob2} \times \Sigma Split_s)$$

$$P_s = (9.69 \times 5.338 \times 4) + 0.3(9.69 \times 5.338 \times 4)$$

$$P_s = 206.9 + 62 = 268.97 \text{ cm} \approx 3 \text{ m}$$

C. **FILTER CAPASITOR OUPUT**

$$\frac{\Delta V_o}{V_o} = \frac{1-D}{8 \times L_x \times C_o \times (2f_s)^2}$$

$$\Delta V_o = \pm 0.1\% \times V_o = 0.001 \times V_o$$

$$\Delta V_o = \pm 0.1\% \times V_o = 0.001 \times 19 = 0.019$$

$$\frac{0.019}{19} = \frac{1-0.4}{8 \times 2.8305 \times 10^{-4} \times C_o \times (2 \times 40k)^2}$$

$$C_o = 4.14017 \times 10^{-5} F$$

$$C_o \approx 42 \mu F$$

Rekomendasi = 47 μF , 50v

- **R and C snubber**

Kondisi off-state(S1)

$$V_{OFF} = V_{C1} - V_{Lx} - V_o$$

$$V_{OFF} = \frac{V_s}{2} - L_x \frac{di_L}{dt} - V_o$$

Kondisi on-State(S1)

$$I_{on} = I_{L(avg)} = I_o$$

$$V_{OFF} = \frac{V_s}{2} - L_x \frac{f \times \Delta i_L}{D} - V_o$$

$$V_{OFF} = \frac{100}{2} - 2.8305 \times 10^{-4} \times \frac{40 \times 10^3 \times 0.6}{0.4} - 19$$

$$V_{OFF} = 14.02 \text{ V}$$

$$I_{on} = I_o = 3 \text{ A}$$

$$T = \frac{1}{f} = \frac{1}{40k} = 0.000025 \text{ s}$$

$$C_{snubber} \approx \frac{I_{on} \times t_{fall}}{2 \times V_{OFF}}$$

$$C_{snubber} = \frac{3 \times 75 \times 10^{-9}}{2 \times 14.02}$$

$$C_{snubber} = 8.024 \times 10^{-9} \text{ F}$$

$$C_{snubber} \approx 9 \text{ nF}$$

$$\text{Rekomendasi: } C_{snubber} = 10 \text{ nF, 1kV}$$

$$R_{snubber} < \frac{DT}{2 \times C_{snubber}}$$

$$R_{snubber} < \frac{0.4 \times 2.5 \times 10^{-5}}{2 \times 8.024 \times 10^{-9}}$$

$$R_{snubber} < 623 \Omega$$

$$R_{snubber} \approx 470 \Omega, 10 \text{ watt}$$

$$\text{rekomendasi: } R_{snubber} = 470 \Omega, 10 \text{ watt}$$